

Homework 1

The pdf you submit must look exactly like this with the answers and all supporting works shown on the the page with the question.

Last Name	First Name	Student ID
Malloy	Sean	998853012
Partner Last Name	Partner First Name	Partner Student ID

1. (5 points) Use Boolean Algebra to prove that

$$y = (A * B * \bar{C}) + (\bar{A} * B * C) + (A * \bar{B} * C) + (A * B * \bar{C}) + (A * B * C) = (A + B) * (B + C) \quad \text{X}$$

SOP to POS

$$(\bar{A} B \bar{C} + \bar{A} B C) + (A \bar{B} C + A B \bar{C}) + A B C = (A + B) * (B + C)$$

taking De Morgan's theorem twice get's us

$$\bar{y} = \bar{A} \bar{B} C + A \bar{B} \bar{C} + \bar{A} B \bar{C} + A \bar{B} C + A B \bar{C}$$

$$\bar{y} = (A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)(\bar{A} + B + C)$$

$$\bar{y} = (\bar{A} + B + \bar{C})(\bar{A} + B + C)(A + \bar{B} + C)(A + B + \bar{C})(A + B + C)$$

$$\text{Distributive} \rightarrow (\bar{A} + (B + \bar{C})(B + C)) (A + (\bar{B} + C)(B + \bar{C})(B + C))$$

$$\text{Combining} (\bar{A} + B) (A + B + C)$$

$$(A + B) * (B + C)$$


A	B	C	y	X
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	0
1	1	0	1	1
1	1	1	1	1

2. (3 points) Prove that $A \text{ XOR } B = A * \bar{B} + \bar{A} * B$

A	B	A XOR B	$A * \bar{B} + \bar{A} * B$
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

These two equations have the same truth tables to each other. Because $A \text{ XOR } B = A * \bar{B} + \bar{A} * B$ for all cases, then perfect induction we can conclude that the theorem is proved.

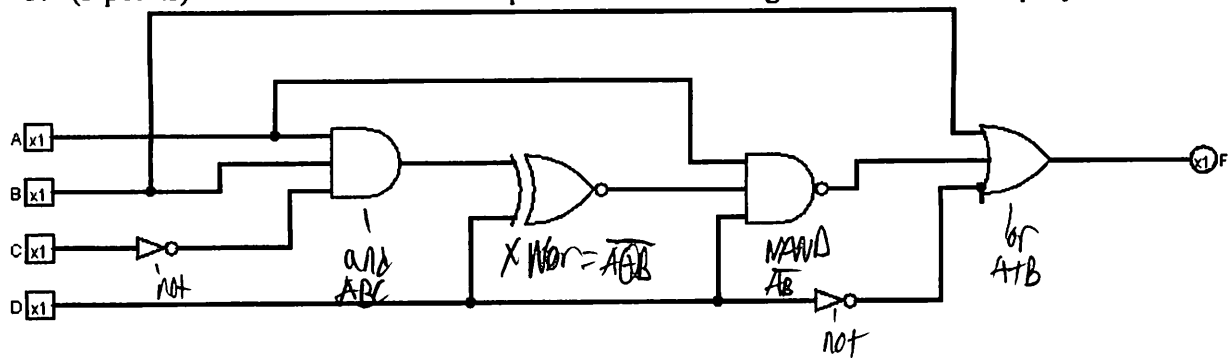3. (3 points) Write the function that represents the following circuit. Do not simplify.



$$\overline{(\overline{ABC} \oplus D)}(A \vee D) + B + \overline{D}$$

4. Given the following truth table

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

1. (3 points) Write a function in SOP form that behaves according to the truth table. Do not simplify.

$$m_0 + m_1 + m_2 + m_5 + m_6$$

$$\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}C + AB\bar{C}$$

2. (3 points) Write a function in POS form that behaves according to the truth table. Do not simplify.

$$M_3 + M_4 + M_7$$

$$(A + \bar{B} + \bar{C})(\bar{A} + B + C)(\bar{A} + \bar{B} + C)$$

5. (3 points each) For each of the following problems assume that the variables are $x_0 - x_{N-1}$, with x_0 representing the least significant bit and x_{N-1} the most significant. For example if we had an equation of 3 variables, $m_1 = \bar{x}_2 * \bar{x}_1 * x_0$ and $m_6 = x_2 * x_1 * \bar{x}_0$. For each of the following problems write each function in **both** its most simplified SOP and POS form. There are a total of 5 subquestions

1. $m_0 + m_1 + m_2$

A	B	$m_0 + m_1 + m_2$
0	0	1
0	1	1
1	0	1
1	1	0

SOP: $(\bar{A}\bar{B}) + (\bar{A}B) + (A\bar{B})$

$\bar{A} + (\bar{B}B) + (A\bar{B})$

↓

$\bar{A} + A\bar{B}$

POS:

$\bar{A} + \bar{B}$

2. $M_0 * M_3 * M_4 * M_7$

A	B	C	M_0	M_3	M_4	M_7
0	0	0	0			
0	0	1	1			
0	1	0	1			
0	1	1	0			
1	0	0	0			
1	0	1	1			
1	1	0	1			
1	1	1	0			

$$\begin{aligned} \text{SOP: } & (\bar{A}\bar{B}C) + (\bar{A}B\bar{C}) + (A\bar{B}C) + (AB\bar{C}) \\ & \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}C + B\bar{C}) \\ & = \boxed{\bar{B}C + B\bar{C}} \end{aligned}$$

$$\text{POS: } (A+B+C)(A+\bar{B}+\bar{C})(\bar{A}+B+C)(\bar{A}+\bar{B}+\bar{C})$$

$$\begin{aligned} & [A + (B+C)(\bar{B}+\bar{C})] [\bar{A} + (B+C)(\bar{B}+\bar{C})] \\ & = \boxed{(B+C)(\bar{B}+\bar{C})} \end{aligned}$$

3. $m_4 + m_5 + m_7 + m_{12} + m_{13} + m_{15}$

4 digits required

Use K map

AB \ CD	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	0	0	0	1

SOP

$$B\bar{C} + BD$$

$$B(\bar{C} + D) \text{ --- Distributive}$$

POS

$$B(\bar{C} + D)$$

4. $m_0 + m_3 + m_4 + m_8 + D_2 + D_5 + D_7 + D_{10} + D_{13} + D_{15}$

AB \ CD	00	01	11	10
00	1	1	0	1
01	1	1	1	0
11	1	1	1	0
10	0	0	0	1

SOP
 $\bar{A}\bar{C} + \bar{A}D + A\bar{B}\bar{D}$

POS

$$(\bar{C} + D)(\bar{A} + \bar{B})(\bar{A} + \bar{D})$$

5. $m_1 + m_3 + m_7 + m_9 + m_{11} + m_{15} + m_{17} + m_{19} + m_{25} + m_{27} + D_4 + D_6 + D_{12}$
 $+ D_{14} + D_{16} + D_{18} + D_{20} + D_{22} + D_{24} + D_{26} + D_{28} + D_{30}$

BC	00	01	11	10
DE	0	0	0	0
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

A=0

SOP

$$\bar{B}\bar{C}B + DE\bar{A} + B\bar{C}B$$

BC	00	01	11	10
DE	0	0	0	0
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

A=1

POS

$$(\bar{D} + E)(\bar{C} + \bar{A})(D + E)(D + \bar{C} + \bar{A})$$